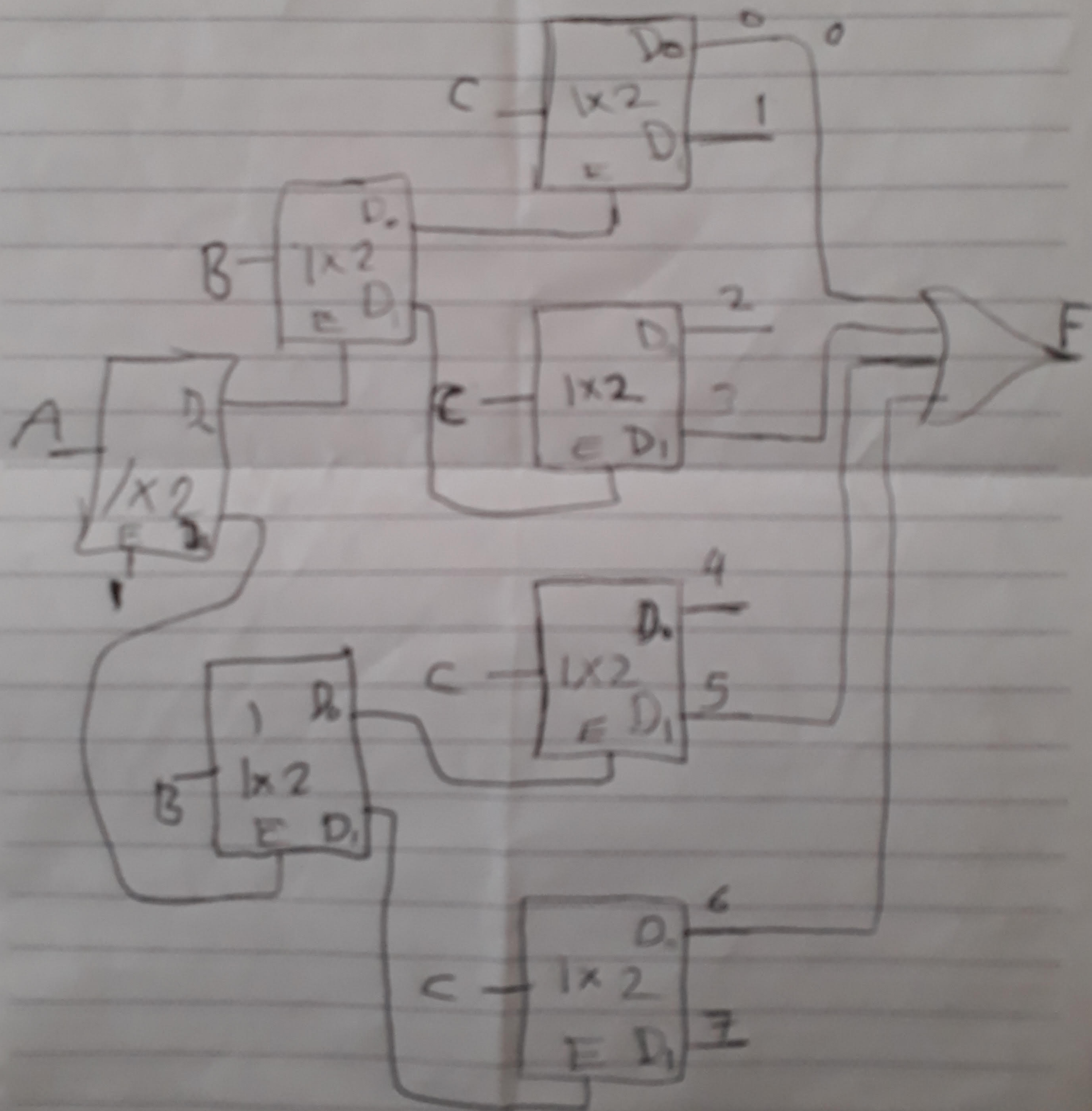


A 3rd

Q: Implement the following function using 1x2 Decoders and OR gate with Active High

$$F(A, B, C) = \sum (0, 3, 5, 6)$$



Ques 1

Q: Implement the following function using only 3x8 Decoders and OR gate.
Active High

$$F(A, B, C, D) = \sum (0, 1, 4, 7, 8, 10, 14)$$

Soln

