

Q1: Implement the following Boolean functions using 8x4 ROM

$$W(a,b,c)=\sum(0, 1, 3, 5, 7), X(a,b,c)=\sum(0, 2, 4, 5), Y(a,b,c)=\sum(1, 2, 4, 7),$$

$$Z(a,b,c)=\sum(0, 3, 5, 6, 7).$$


(4 Marks)

Q2: Implement a Full Adder, using **two** 4x1 Multiplexers (connect **x** and **y** as Selection lines).

(6 Marks)

Q3: For the following state diagram use this state assignments, design a system using **D** flip flops.

(10 Marks)

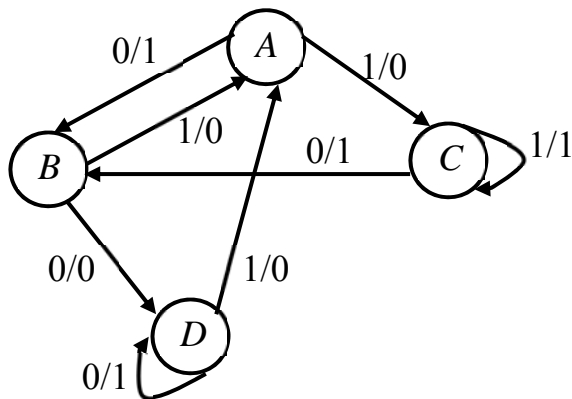

q	q_1	q_2
A	0	0
B	1	1
C	1	0
D	0	1

Q1: Implement the following Boolean functions using 8x4 ROM

$$W(a,b,c)=\sum(0, 1, 3, 5, 7), X(a,b,c)=\sum(0, 2, 4, 5), Y(a,b,c)=\sum(1, 2, 4, 7),$$

$$Z(a,b,c)=\sum(0, 3, 5, 6, 7).$$


(4 Marks)

Q2: Implement a Full Adder, using **two** 4x1 Multiplexers (connect **x** and **y** as Selection lines).

(6 Marks)


Q3: For the following state diagram use this state assignments, design a system using **D** flip flops.

(10 Marks)

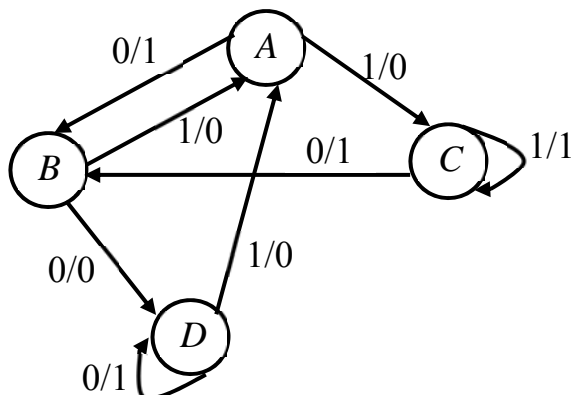

q	q_1	q_2
A	0	0
B	1	1
C	1	0
D	0	1

Q1:

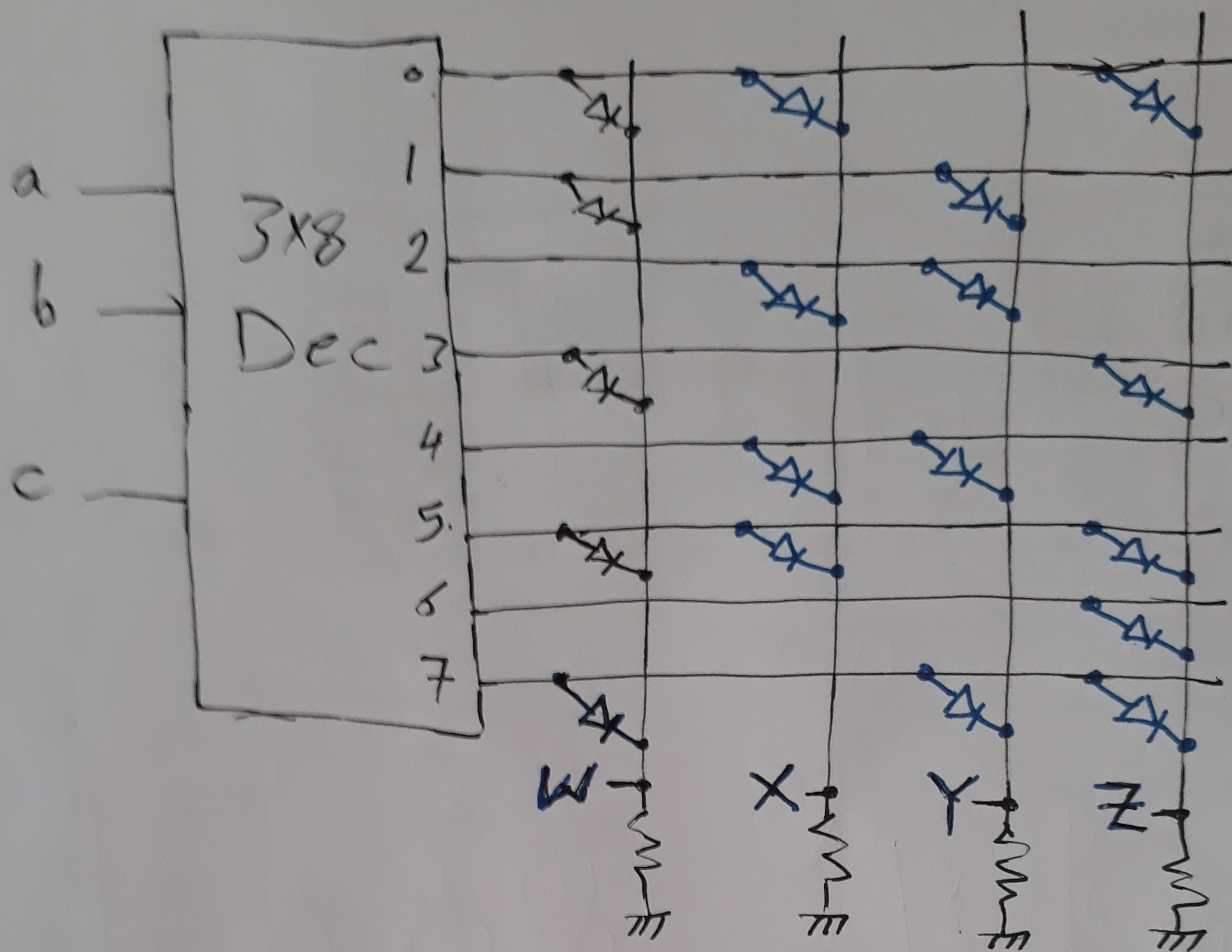

(3)

The Data at address 2 is 0 1 1 0
 = = = = 6 is 0 0 0 1

(1)

Q 2:

x	y	z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

For S (Sum) = $\sum(1, 2, 4, 7)$


$$I_0 = \bar{x}\bar{y}, I_1 = \bar{x}y$$

$$I_2 = x\bar{y}, I_3 = xy$$

	I_0	I_1	I_2	I_3
\bar{z}	0	(2)	(4)	6
z	(1)	3	5	(7)
	z	\bar{z}	\bar{z}	z

For C (carry) = $\sum(3, 5, 6, 7)$

	I_0	I_1	I_2	I_3
\bar{z}	0	2	4	(6)
z	1	(3)	(5)	(7)
	0	z	z	1

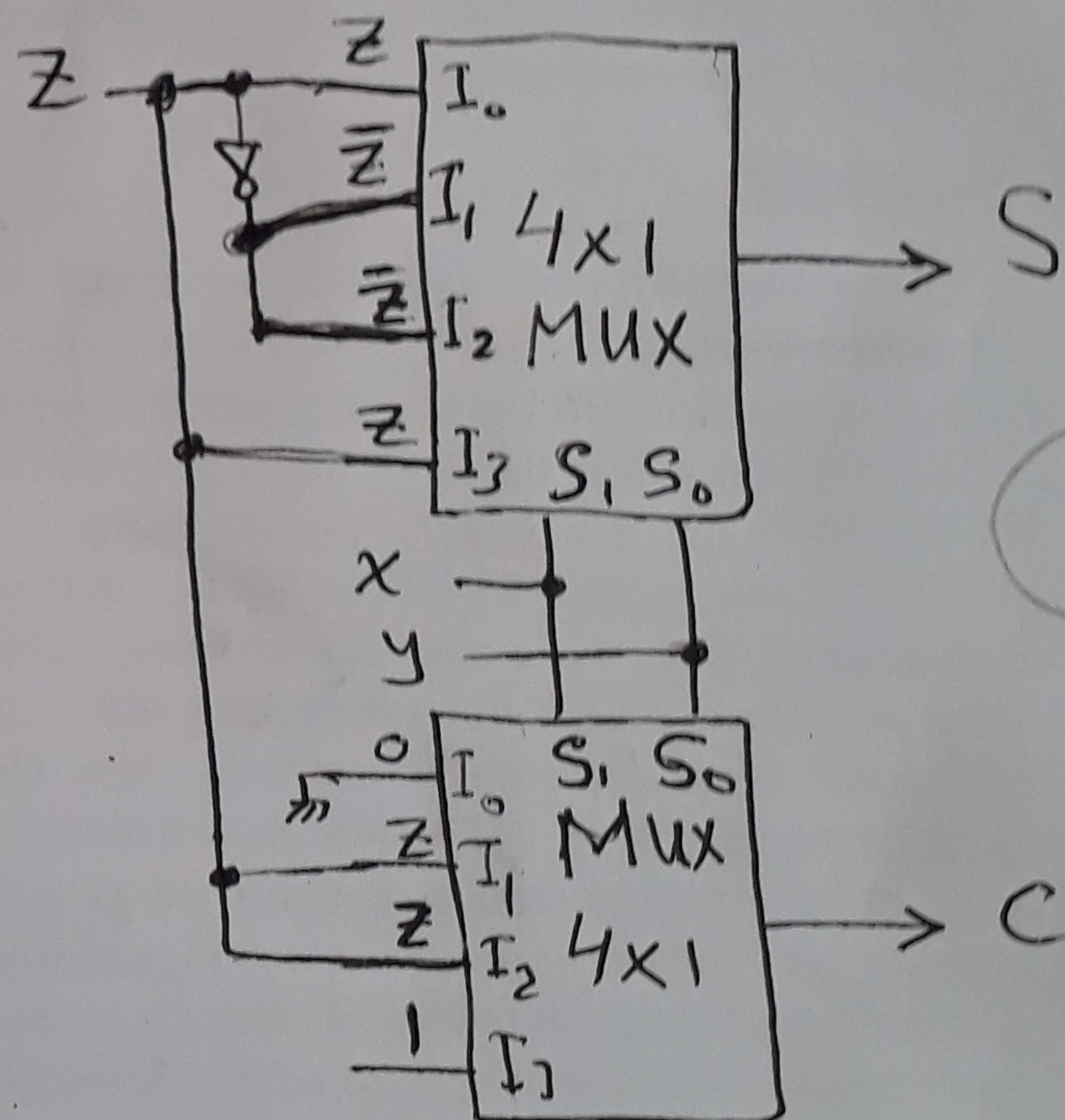

Q3:

P.S	N.S		O/P Z	
	$x=0$	$x=1$	$x=0$	$x=1$
A	B	C	1	0
B	D	A	0	0
C	B	C	1	1
D	D	A	1	0

(2)

(1)

P.S	N.S		O/P
	q_1	q_2	
A	0	0	0
B	1	1	0
C	1	0	0
D	0	1	0

(2)

P.S	N.S		O/P
	q_1	q_2	
A	1	1	1
B	0	1	0
C	1	0	1
D	0	0	1

(1)

$q_1 q_2$	00	01	11	10
x	1			1
	1			1

\bar{q}_1 q_1

\bar{q}_2 q_2 \bar{q}_2

$D_1 = \bar{q}_2$

(1)

$q_1 q_2$	00	01	11	10
x	1	1	1	1

$D_2 = \bar{x}$

(1)

$q_1 q_2$	00	01	11	10
x	1	1		1
				1

$Z = q_1 \bar{q}_2 + \bar{q}_1 \bar{x}$

