



2019 - 2018

Max. Mark: 100%

Notes: ANSWER FOUR QUESTIONS.

Using Scientific Calculator is **NOT** Allowed


Q1: A Half Adder (H.A) is a circuit that adds two bits to give a sum and a carry. Give the truth table for a Half Adder, and design the circuit using only two gates. Then design a combinational circuit that converts a four-bit Gray code to a four-bit Binary number. Use only Half Adder blocks (H.A's). (25 Marks)

Q2: A) Given $F = A\bar{B}\bar{D} + \bar{A}B + \bar{A}C + CD + ABC\bar{D}$. Use Karnaugh map to find

- I. The minimum SOP expression for F . (5 Marks)
- II. The minimum POS expression for F . (5 Marks)

Q2: B) For the circuit shown below:

(15 Marks)

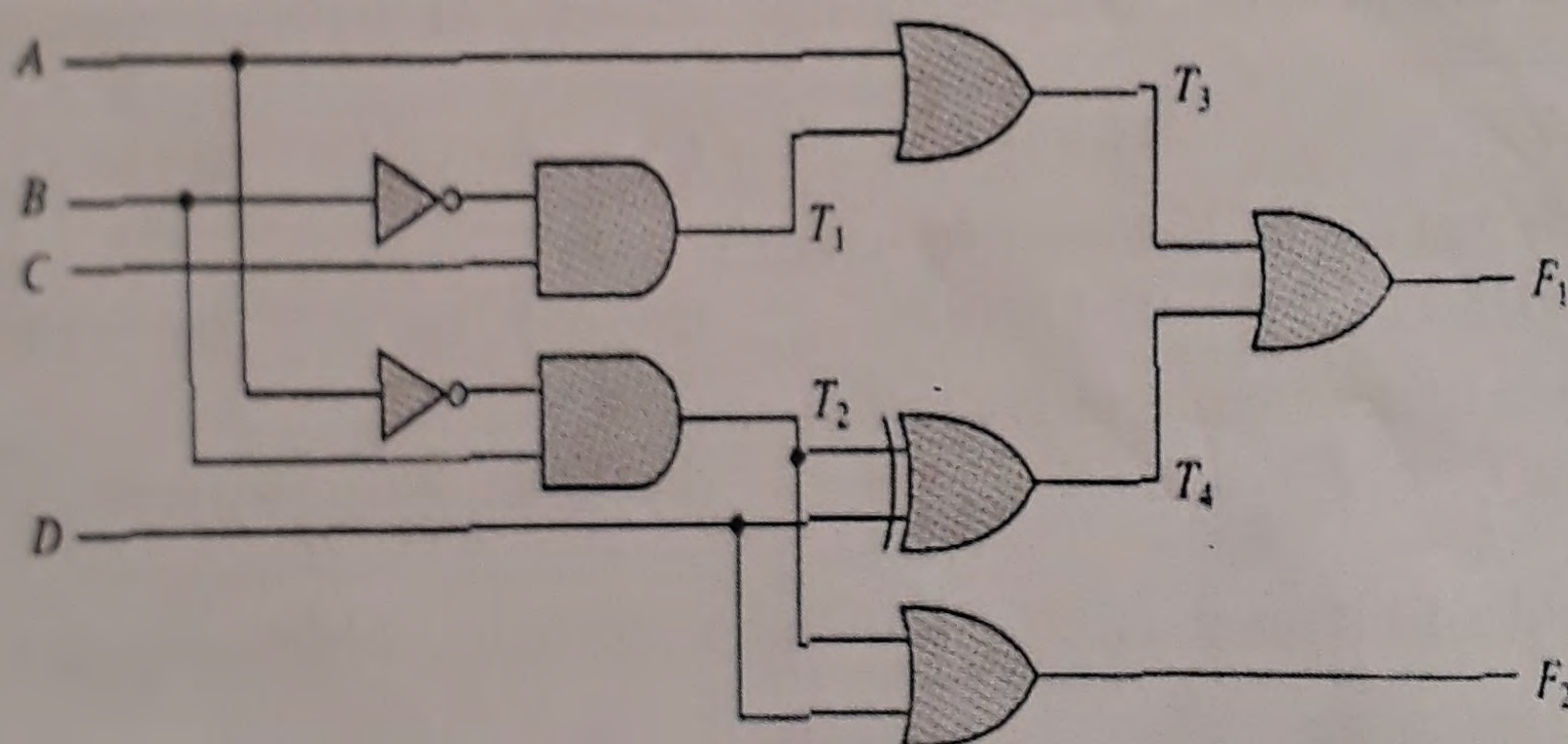

- i- Derive the Boolean expression for T_1 , T_2 , T_3 , and T_4 . Evaluate the outputs F_1 and F_2 as a function of the four inputs.
- ii- List the truth table of the four input variables, then list the binary values for T_1 , T_2 , T_3 , T_4 and outputs F_1 and F_2 in the table.
- iii- Plot the Boolean output functions obtained in part (ii) on maps, and show that the simplified Boolean expressions are equivalent to the ones obtained in part (i).

Q3: A) If $(10n01)_2 = (33)_r$. Find both n and r . (12 Marks)

Q3: B) Implement the following Boolean function $f(a, b, c, d) = \sum(0, 1, 2, 4, 6, 10, 12, 14)$ using 4x1 Multiplexer, choose a and d as select lines. (13 Marks)

Q4: Choose the right answer (only one choice):

(25 Marks)

1. The result of $(23B)_{12} + (A87)_{12} = \text{-----}$.

- A) $(CC5)_{12}$ B) $(1106)_{12}$ C) $(DB2)_{12}$ D) $(10B6)_{12}$.

2. ----- is the 9's complement of the number $(465)_9$.

- A) $(423)_9$ B) $(424)_9$ C) $(534)_9$ D) $(535)_9$.

3. The result of $(221)_3 - (102)_3 = \text{-----}$.

- A) $(119)_3$ B) $(111)_3$ C) $(112)_3$ D) $(122)_3$.

4. In 5-variable Karnaugh map, a 3-variable product term is produced by

- A) a 16-cell group of 1's B) an 8-cell group of 1's
C) a 4-cell group of 1's D) a 2-cell group of 1's

5. The EX-OR operation can be produced with

- A) Two NAND gates B) Three NAND gates
C) Four NAND gates D) Five NAND gates

6. In the 2's complement form, the binary number (10110101) is equal to the decimal number -----.

- A) -75 B) +181 C) +75 D) -53

7. The code that has an Even-parity error is -----.

- A) 1010011 B) 1101011 C) 1001010 D) 1110101

8. According to the commutative law of addition,


- A) $X+Y=Y+X$ B) $X+\bar{X}=1$ C) $X+(Y+Z)=(X+Y)+Z$ D) $X+0=X$

Q5: A) Build a 4-bit magnitude Comparator, using only 2-bit magnitude Comparators. (15 Marks)

Q5: B) Show how to configure each of the following two-input devices as an inverter:

- i. Two input NOR. (5 Marks)
ii. Two input Ex-OR. (5 Marks)

Good Luck
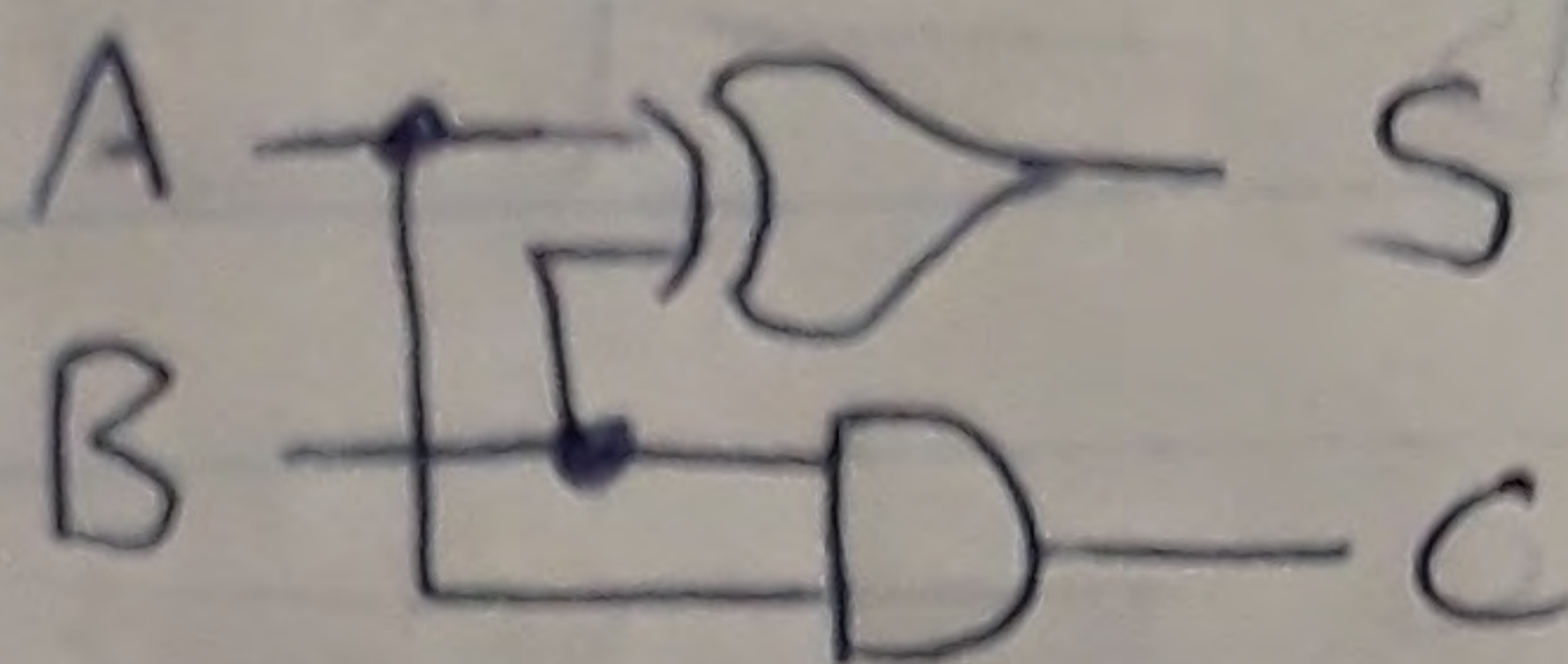
$$C \equiv A.B$$


$\overline{A}$ A

AB	$\overline{A}$	A
00	00	11
01	01	10
11		
10		

$\overline{B}$ B $\overline{B}$

$$W = A$$

AB

CD

	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

$$X = \bar{A}B + A\bar{B} = \boxed{A \oplus B}$$

Q. 6

Construct truth table for the following function:

$$F(A, B, C) = \sum(0, 1, 2, 4, 7)$$

Solution:

	AB	$\bar{A}$		A		
		00	01	11	10	
$\bar{C}$	00		1		1	D
	01		1		1	
C	11	1		1		D
	10	1		1		

$$y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$


$$y = A \oplus B \oplus C$$

AB

CD	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

$$\underline{Z = A \oplus B \oplus C \oplus D}$$

(2)

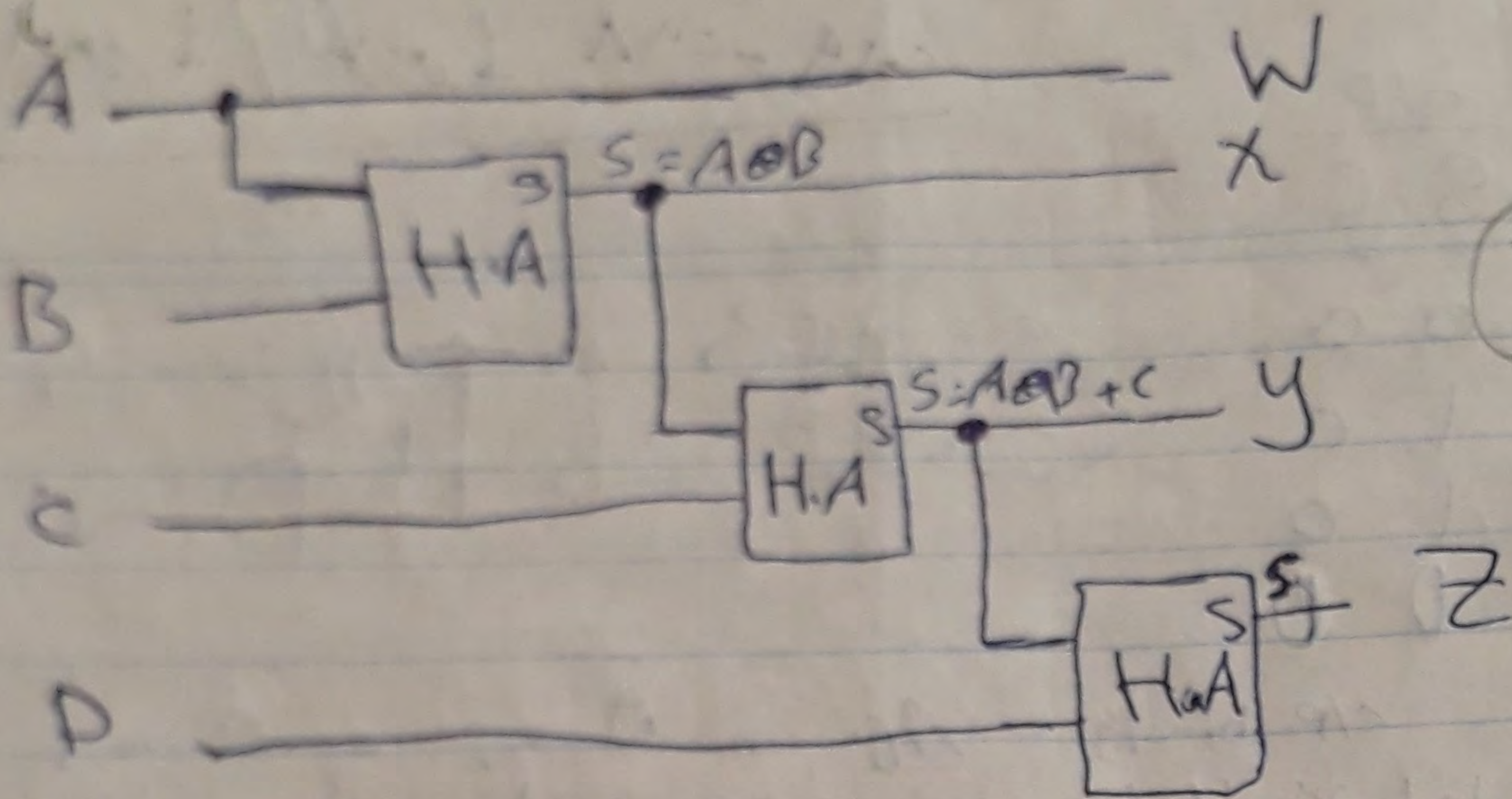

(3)

Q2: A) $F = A\bar{B}\bar{D} + \bar{A}B + \bar{A}C + CD + ABC\bar{D}$

I)

AB		$\bar{A}$				A	
		00	01	11	10		
$\bar{C}$	00	0	1	0	1	D	
	01	0	1	0	0		
C	11	1	1	1	1	$\bar{D}$	
	10	1	1	1	1		
		$\bar{B}$		B		$\bar{B}$	

(3)

$$F = A\bar{B}\bar{D} + \bar{A}B + C$$

(3)

II) $\bar{F} = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{C}D$

$$F = (A+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+C+\bar{D})$$

OR $F = (A+B+C)(\bar{A}+\bar{B}+C)(\bar{B}+C+\bar{D})$

(4)

3

Q2: B) i-) $T_1 = \bar{B}C$, $T_2 = \bar{A}B$

$T_3 = A + T_1 \Rightarrow T_3 = A + \bar{B}C$ (1)

$T_4 = D \oplus T_2 \Rightarrow T_4 = \bar{D}T_2 + D\bar{T}_2$

$= \bar{D}\bar{A}B + D(\overline{\bar{A}B})$

$T_4 = \bar{A}B\bar{D} + AD + \bar{B}D$ (1)

$F_1 = T_3 + T_4 \Rightarrow F_1 = A + \bar{B}C + \bar{A}B\bar{D} + AD + \bar{B}D$

$F_1 = A + B\bar{D} + \bar{B}D + \bar{B}C$ (2)

$F_2 = T_2 + D \Rightarrow F_2 = \bar{A}B + D$ (1)

ii- ^{2/P}

A	B	C	D	T ₁	T ₂	T ₃	T ₄	F ₁	F ₂
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1	1
0	0	1	0	1	0	1	0	1	0
0	0	1	1	1	0	1	1	1	1
0	1	0	0	0	1	0	1	1	1
0	1	0	1	0	1	0	0	0	1
0	1	1	0	0	1	0	1	1	1
0	1	1	1	0	1	0	0	0	1
1	0	0	0	0	0	1	0	1	0
1	0	0	1	0	0	1	1	1	1
1	0	1	0	1	0	1	0	1	0
1	0	1	1	1	0	1	1	1	1
1	1	0	0	0	0	1	0	1	0
1	1	0	1	0	0	1	1	1	1
1	1	1	0	0	0	1	0	1	0
1	1	1	1	0	0	1	1	1	1

(1) (1) (1)

ii)

	AB	$\bar{A}$		A		
		00	01	11	10	
C	$\bar{C}$	00	1	1	1	$\bar{D}$
	01	1		1	1	D
C	11	1		1	1	$\bar{D}$
	10	1	1	1	1	$\bar{D}$
		$\bar{B}$	B		$\bar{B}$	

$F_1 = A + B\bar{D} + \bar{B}C + \bar{B}D$

	AB	$\bar{A}$		A		
		00	01	11	10	
$\bar{C}$	00		1			$\bar{D}$
	01	1	1	1	1	D
C	11	1	1	1	1	D
	10		1	1	1	$\bar{D}$
		$\bar{B}$	B		$\bar{B}$	

$$F_2 = D + \bar{A}B$$

Q 30. A) $(10n01)_2 = 2^4 + n \times 2^2 + 1 = 17 + 4n = 3r + 3$

If $n=0$, then $r = (17-3)/3$ is not an integ

If $n=1$, then $r = (21-3)/3 \Rightarrow r=6$

$$(10101)_2 = (33)_6 = (21)_{10}$$

5

البرور 1 / الكويش 1 - 118 - 119

Q38B) $F = \sum(0, 1, 2, 4, 6, 10, 12, 14)$

$I_0 = \bar{a}\bar{d}$, $I_1 = \bar{a}d$, $I_2 = a\bar{d}$, $I_3 = ad$

	I_0	I_1	I_2	I_3
$\bar{b}\bar{c}$	0	1	8	9
$\bar{b}c$	2	3	10	11
$b\bar{c}$	4	5	12	13
bc	6	7	14	15

$\bar{b}c + b\bar{c} + bc$

$\bar{b}c + b$

$b + c$


$1 \quad \bar{b}\bar{c} \quad b+c \quad 0 \quad 1$

1

1


1

3

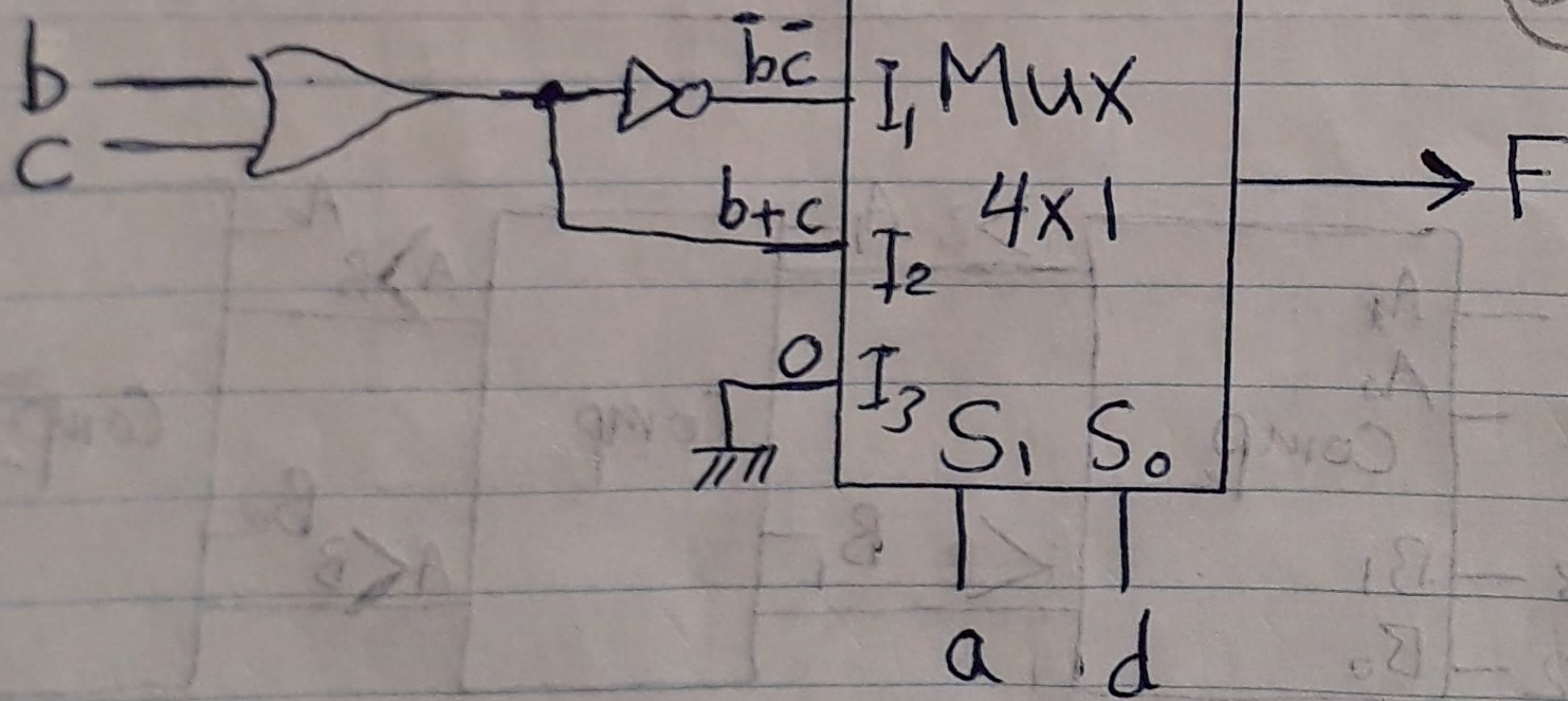


$\bar{A} = \bar{A} \cdot \bar{A} = \bar{A} + A$

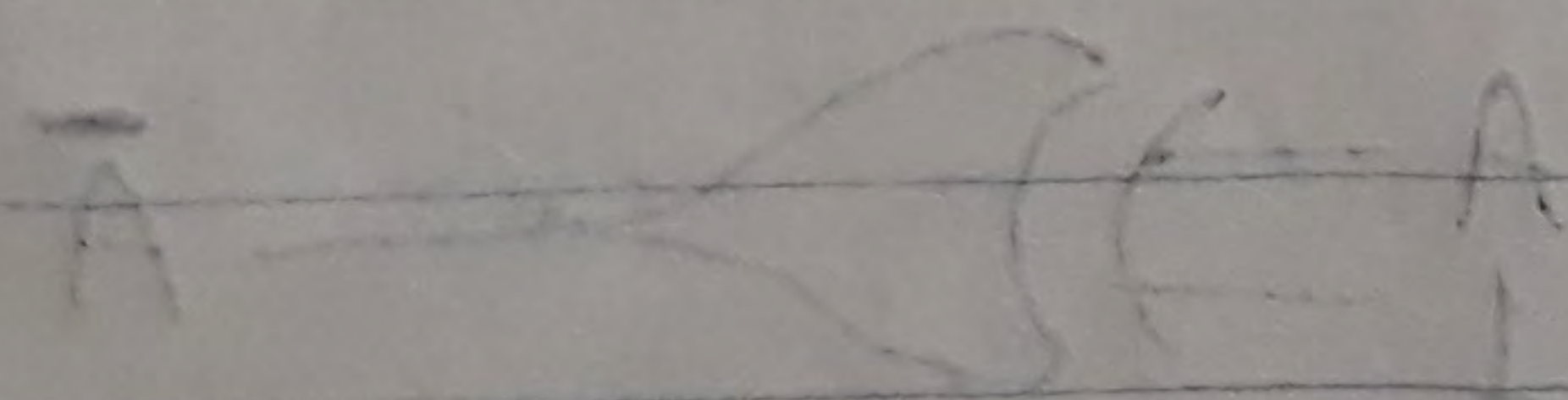$\bar{A} = 1 \cdot \bar{A} + 0 \cdot A = \bar{A} + 0$




- ⑥
- Q4:
- 1- B ②
 - 2- B ⑦
 - 3- C ②
 - 4- C ③
 - 5- D ③
 - 6- A ③
 - 7- A ③
 - 8- A ③

Q5: A)

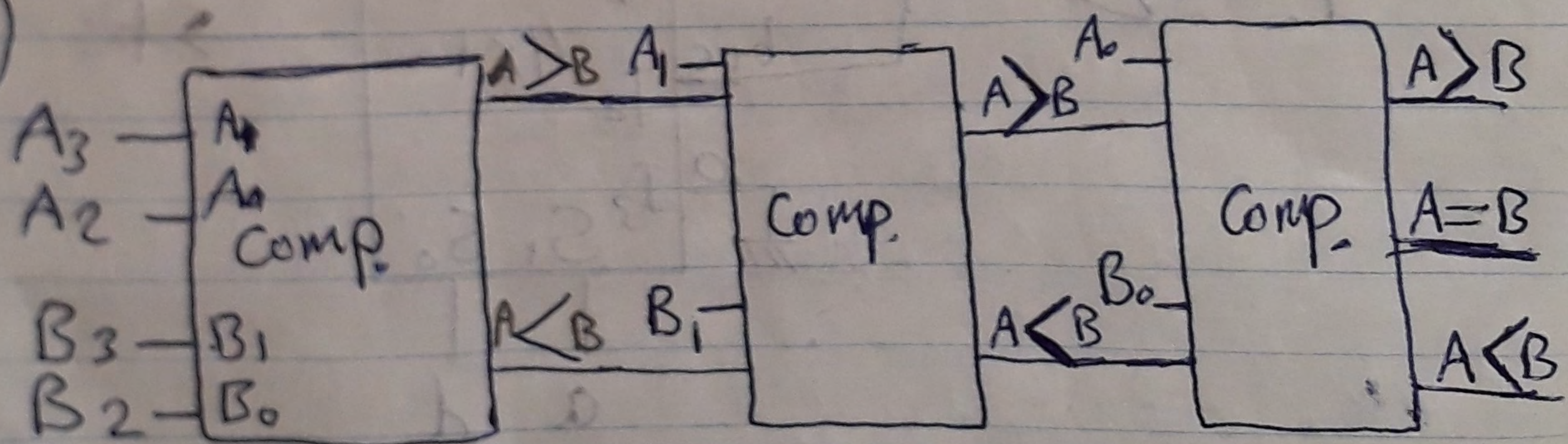

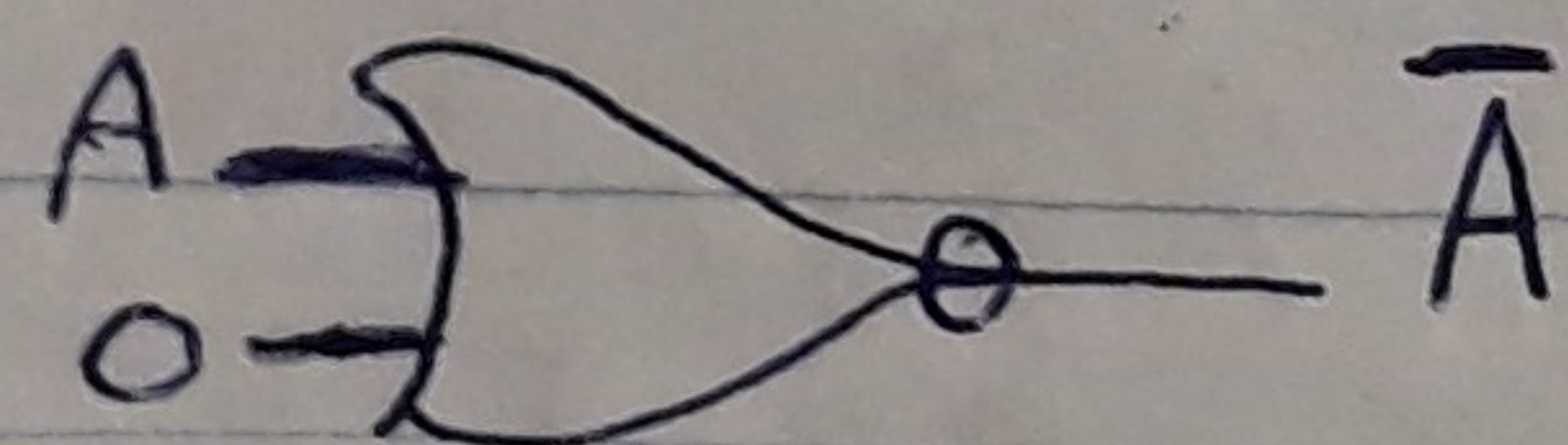Q5: B) i - $\overline{A+B} = \bar{A} \cdot \bar{B} = \bar{A}$



ii - $A\bar{B} + \bar{A}B = A \cdot \bar{1} + \bar{A} \cdot 1 = \bar{A}$

